

# Automotive Technology

## Wiring Diagram Practice 5

Name \_\_\_\_\_ Date \_\_\_\_\_ Period \_\_\_\_\_

Solve the maze using a highlighter marker making no mistakes!

